


PH435 Assignment 1

Sankalp Gambhir

180260032

August 25, 2020

1.

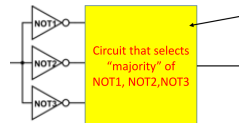

Note: this circuit must be highly optimized with minimum number of parts! You don't want a bit flip to happen in here!

Design a minimal circuit that goes into the yellow box above. It must take 3 digital inputs, and produce 1 digital output. Output = value that matches at least two of the inputs. i.e. Output is the 'majority value' of the 3 inputs. Even if one of the inputs is wrong due to SEU, we will still get the correct answer. [30]

We can construct a simple minimal logic circuit using a Karnaugh Map. First, we establish the form of the circuit and construct a target truth table.

Figure 1: Expected Circuit

And, the truth table for $f(A, B, C)$

A	B	C	$f(A, B, C)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Minimizing f using a Karnaugh Map

we get $f(A, B, C) = AB + BC + CA$.

2. Optimize the layout of the circuit on a 2D silicon wafer to minimize the surface area. The smaller the 2-D surface area, the lesser the probability of the circuit being hit by a cosmic ray particle.

Use the basic source-gate-drain structure of a MOSFET as discussed in class.

[70]

		AB			
		00	01	11	10
C	0	0	0	1	0
	1	0	1	1	1